

Answer all 10 questions. Write your answers in the space provided on the question paper. Anything written on the reverse side won't be marked.

Authorized Memoranda: One crib sheet allowed per student; maximum letter-size paper. Crib sheet can be filled on both sides. Calculators are NOT allowed.

Name:

Student No.:

Section:

Instructors

Pavan Gunupudi

Maitham Shams

Question	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	Q9	Q10	Total
Marks											

1. Find the inverse for the following functions such that there are bars only on single letters. 4 Marks

$$\begin{aligned} \text{(a) } \overline{ab(\overline{cd} + e)} &= \overline{ab} + (\overline{cd} + e) \\ &= \overline{a} + \overline{b} + \overline{c} + \overline{d} + e \end{aligned}$$

$$\begin{aligned} \text{(b) } \overline{(a+b)(\overline{c+d}) + \overline{e}} &= \overline{(a+b)(\overline{c+d})} \cdot e = \overline{[(a+b) + (c+d)]} e \\ &= (\overline{a} + \overline{b} + c + d) e \end{aligned}$$

2. Perform conversion between number systems and fill out the empty boxes. All numbers are unsigned. Each entry in this question will be marked independently. 9 Marks

Binary	Octal	Decimal	Hex
1101110.1	156.4	110.5	6E.8
110101101.11	655.6	429.75	1AD.C
11001000.01	310.2	200.25	C8.4

3. Let $A = 01100010 = (+98)_{10}$, $B = 11011101 = (-35)_{10}$ in 8-bit 2's complement system. Perform the following operations to obtain the 8-bit answers and indicate if there is an overflow (i.e. answer not valid).

8 Marks

(a) $A - B$

$$\begin{array}{r}
 01100010 \\
 00100011 \\
 \hline
 10000101
 \end{array}
 \qquad
 \begin{array}{r}
 98 \\
 -(-35) \\
 \hline
 133
 \end{array}$$

overflow

(b) $A + B$

$$\begin{array}{r}
 01100010 \\
 11011101 \\
 \hline
 00111111
 \end{array}
 \qquad
 \begin{array}{r}
 98 \\
 -35 \\
 \hline
 63
 \end{array}$$

no overflow

(c) $B - A$

$$\begin{array}{r}
 11011101 \\
 10011110 \\
 \hline
 01111011
 \end{array}
 \qquad
 \begin{array}{r}
 -35 \\
 -98 \\
 \hline
 -133
 \end{array}$$

overflow

(d) $B + B$

$$\begin{array}{r}
 11011101 \\
 11011101 \\
 \hline
 10111010
 \end{array}
 \qquad
 \begin{array}{r}
 -35 \\
 -35 \\
 \hline
 -70
 \end{array}$$

no overflow

4. Simplify the following expressions using Boolean algebra.

10 Marks

(a) $z = \bar{a}d\bar{c} + \bar{a}bd + abd + a\bar{b}\bar{c}d + \bar{b}cd$ to 1 literal

$$\begin{aligned}
 &= d(\bar{a}\bar{c} + \bar{a}b + ab + a\bar{b}\bar{c} + \bar{b}c) \\
 &= d[\bar{a}\bar{c} + (\bar{a}+a)b + (a\bar{c}+c)\bar{b}] \\
 &= d(\bar{a}\bar{c} + b + (a+c)\bar{b}) = d(\bar{a}\bar{c} + b + a+c) \\
 &= d(\bar{a} + b + a + c) = d
 \end{aligned}$$

(b) $z = (x+z)(w+y) + wxz$ to 4 literals

$$\begin{aligned}
 z &= xw + xy + zw + zy + wxz \\
 &= xw(1+z) + xy + zw + zy \\
 &= xw + xy + zw + zy = x(w+y) + z(w+y) \\
 &= (x+z)(w+y)
 \end{aligned}$$

5. Use exhaustive proof to show whether the following equations are valid.

6 Marks

(a) $\overline{a+b+c} = \bar{a}\bar{b}\bar{c}$

abc	$\overline{a+b+c}$	$\bar{a}\bar{b}\bar{c}$
000	1	1
001	0	0
010	0	0
100	0	0
101	0	0
110	0	0
111	0	0

valid.

(b) $\overline{ab+c} = \bar{a} + \bar{b}\bar{c}$

abc	$\overline{ab+c}$	$\bar{a} + \bar{b}\bar{c}$
000	1	1
001	0	1
010	1	1
011	0	1
100	1	1
101	0	0
110	0	0
111	0	0

not valid.

6. Write the duals of the following expressions such that there are bars only on single letters.

4 Marks

(a) $\{ \bar{a}\bar{b} + \bar{c}a + bc \}$

dual $\rightarrow (a+\bar{b})(\bar{c}+a)(b+c)$

(b) $\{ ab(\bar{c}d + e) \}$

dual $\rightarrow \{ a+b + (\bar{c}d + e) \} = a+b + \overline{(\bar{c}d + e)}$
 $= a+b + \overline{\bar{c}d} + \bar{e} = a+b + \bar{c}\bar{d} + \bar{e}$

7. Prove the following identities using Boolean algebra.

9 Marks

(a) Distributive Law: $XY + Z = (X + Z)(Y + Z)$

$$\begin{aligned} \text{RHS} &= (X + Z)(Y + Z) = XY + XZ + ZY + Z \cdot Z \\ &= XY + XZ + ZY + Z = XY + (X + Y + 1)Z \\ &= XY + Z = \text{LHS} \end{aligned}$$

(b) Consensus Theorem: $XY + YZ + \bar{X}Z = XY + \bar{X}Z$

$$\begin{aligned} \text{LHS} &= XY + YZ \cdot 1 + \bar{X}Z \\ &= XY + YZ(X + \bar{X}) + \bar{X}Z \\ &= XY + YZ X + YZ \bar{X} + \bar{X}Z \\ &= XY(1 + Z) + \bar{X}Z(Y + 1) \\ &= XY + \bar{X}Z \end{aligned}$$


(c) $(\bar{X} + Z)(X + Y)(X + Z) = Z(X + Y)$

$$\begin{aligned} \text{LHS} &= (\bar{X}X + \bar{X}Z + ZX + Z\bar{X})(X + Y) \\ &= (\bar{X}Z + ZX + Z)(X + Y) \\ &= Z(X + Y) = \text{RHS} \end{aligned}$$

8. Draw the simplest logic gate or circuit for the following descriptions. The inputs are a, b, c and the output is z .

(a) $z = 1$ only when $abc = 110$

2 Marks

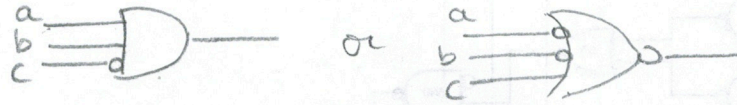


(b) $z = 0$ only when $abc = 010$

2 Marks




(c) $z = 0$ if $abc = 010$ or $abc = 111$

3 Marks

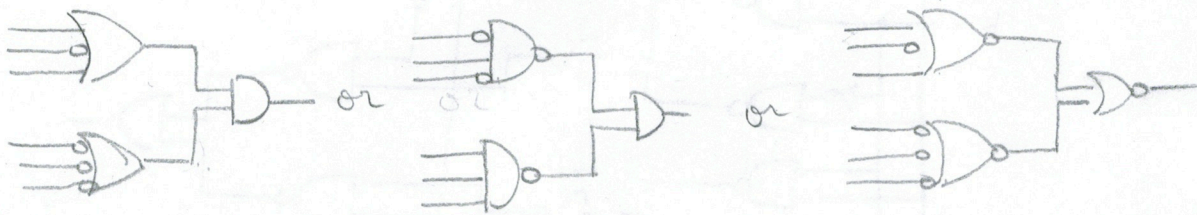


and several other alternatives

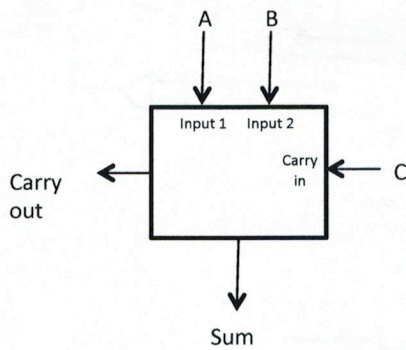9. A 3-input full adder is being tested in a simulation. The following figure shows the waveforms for the inputs A, B and C. Determine the correct values of the output waveforms for Carry and Sum. 8 Marks





3-input full adder

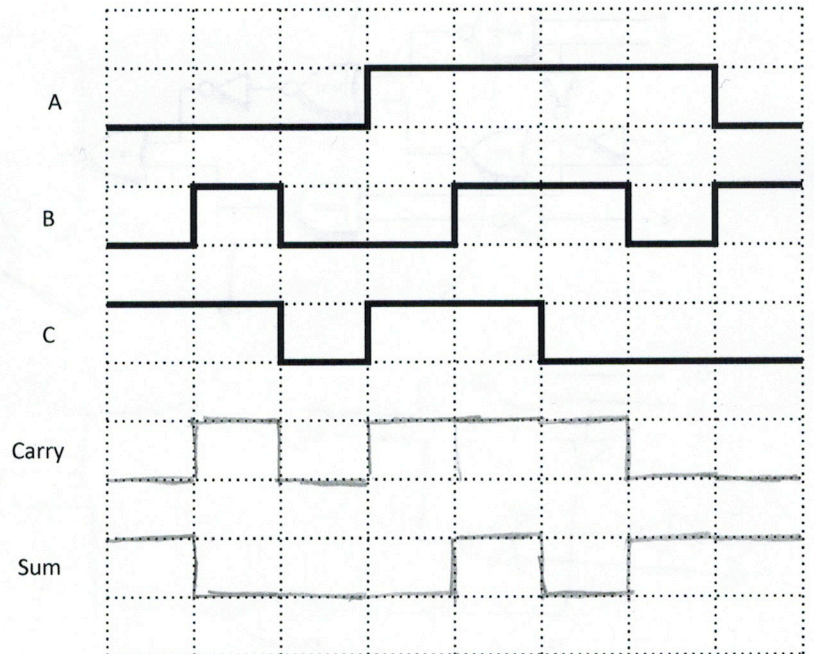

10. (a) Convert the following AND-OR circuit to a circuit consisting of only 2-input NAND gates and inverters (bubbles not allowed).

6 Marks

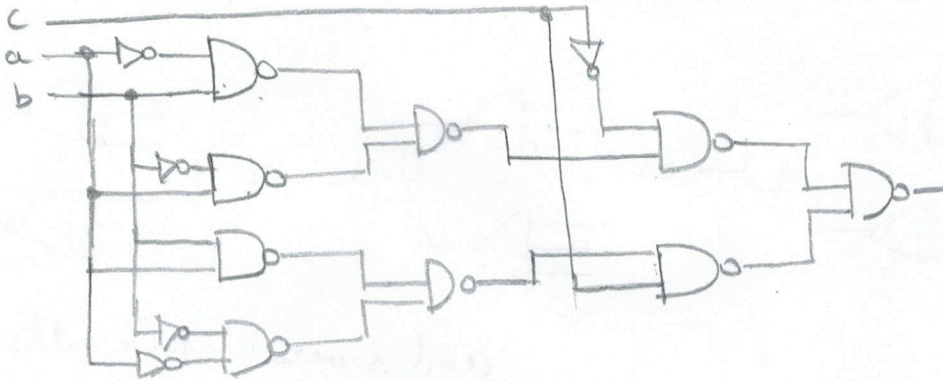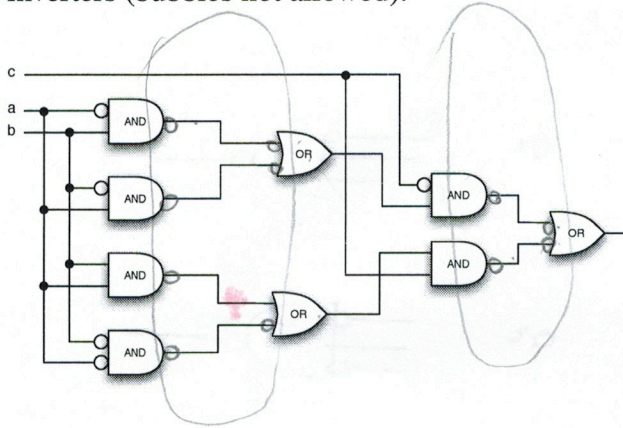

- (b) Convert the following NAND-NOR circuit to an AND-OR circuit (bubbles allowed). Skip the first and third layer during conversion.

4 Marks

